



CURRENT-MODE ELECTRONIC INTERFACES FOR  
SENSOR APPLICATIONS

Giuseppe Ferri  
Gianluca Barile

University of L'Aquila, DIIE

ELECTRONICS FOR SENSORS  
&  
BIOMEDICAL APPLICATIONS  
TECHNOLOGIES & SENSORS  
JOINT WORKSHOP

2020

# OUTLINE

---



01.

## SENSORS, A QUICK RECAP

What is a sensor? How can it be characterized?

02.

## ELECTRONIC INTERFACES

Why using an electronic interface? Discrete vs integrated?

03.

## CURRENT MODE APPROACH

How can we define the concept of current mode operation? What are the main active current mode devices?

04.

## THE SECOND GENERATION VOLTAGE CONVEYOR

The VCII, theory of operation, advantages and disadvantages versus CCIs and Op-Amps.

05.

## VCII BASED INTERFACES FOR SiPMs

How can we take advantage of a VCII for interfacing a current-emitting device.

06.

## VCII BASIC INTEGRATED TOPOLOGIES



Some transistor level designs.

The UnivAQ logo features the text "UnivAQ" in a dark grey, sans-serif font. The letters "A" and "Q" are partially enclosed by a yellow, stylized shield-like shape that has a pointed top and bottom.




# SENSORS, A QUICK RECAP
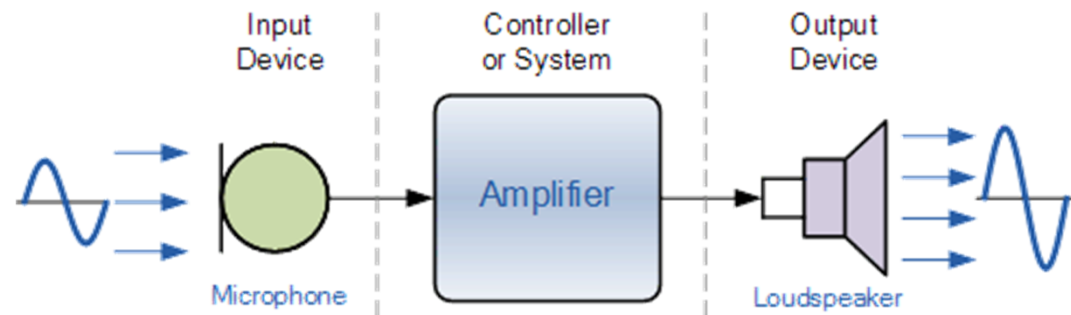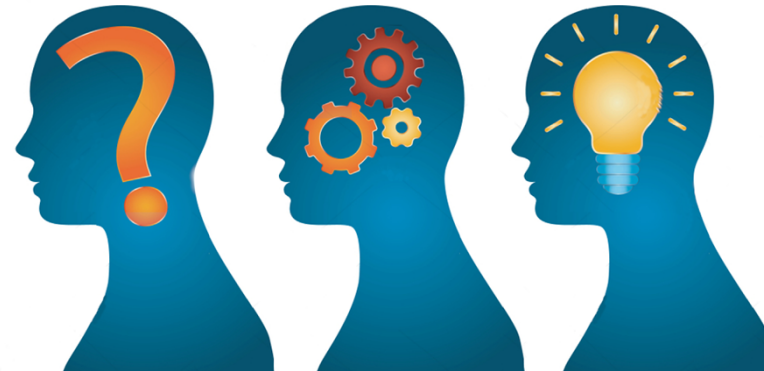
# Introduction

- Interaction between living beings requires **SENSING**, **DECISIONS** and **ACTIONS**.
- Natural phenomena are often characterized by **physical, chemical or biological events**. In order to detect and quantify these events, we need a device or an instrument, to be inserted as first and main element in measurements and control systems. It is the sensing element, in a revelation equipment, which reacts to the phenomenon to be detected.



# Some definitions

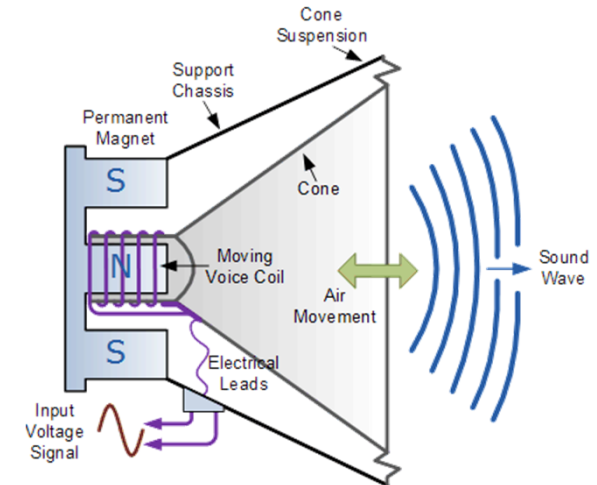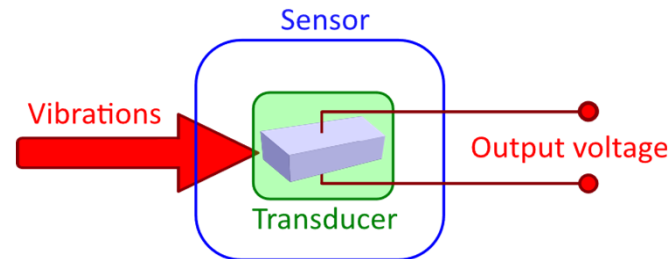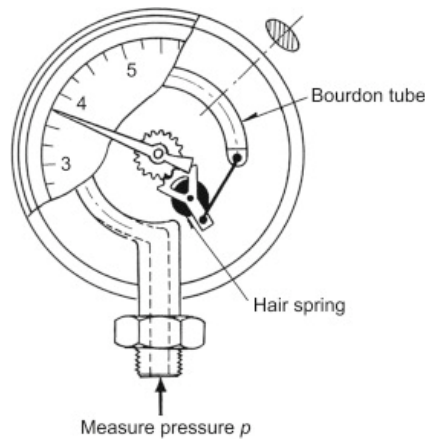

**TRANSDUCERS:** convert signals from one energy domain into signals in a different energy domain.



**SENSORS:** convert signals from an energy domain into ELECTRICAL signals.

**ACTUATORS:** convert electrical signals into non-electrical signals.

**SMART SYSTEMS** both bring the measured information from non-electrical domain into electrical and take the actuation decision back, toward the non-electrical domain, making use of sensors and actuators.
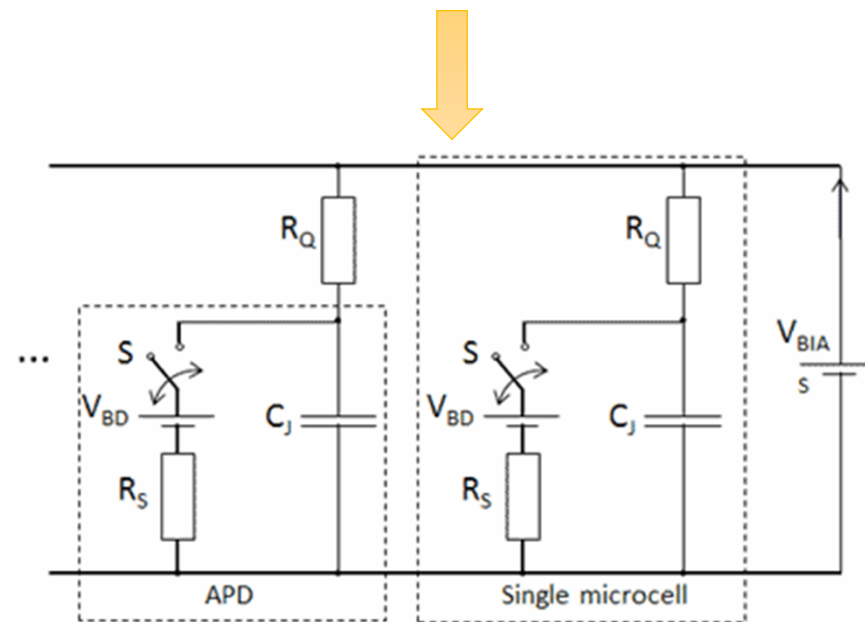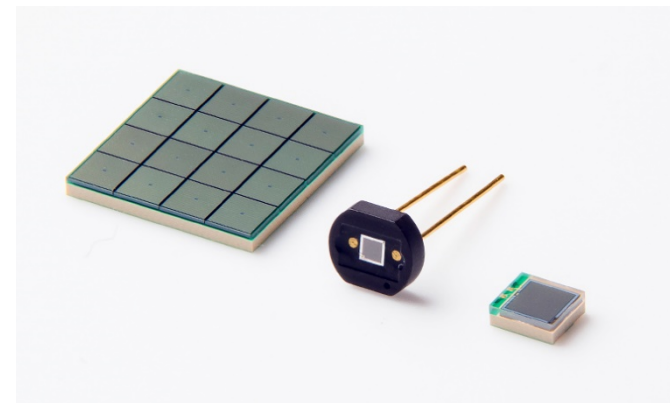
# Sensor modelling


- Generally sensors don't give directly a readable signal. The majority of the sensors are **PASSIVE** elements, that can be modelled by a **resistor** or a **capacitor**, and vary their parameters according to the change of the biological/chemical/physical measurand variation.
- For this reason, an accurate **modelling** ("analog behavioural model") of the sensor behaviour must be performed.
- Since a better electrical signal to be quantified is a **current or a voltage**, the sensor can be **BIASED**. Its output signal often is quite low and must be typically amplified so to have a sufficient reading level.



The UnivAQ logo features the text "UnivAQ" in a dark grey, sans-serif font. The letters "A" and "Q" are significantly larger than the other letters. A yellow shield-like outline is positioned behind the "A" and "Q", with its top and bottom points extending above and below the letters respectively.

UnivAQ

# ELECTRONIC INTERFACES


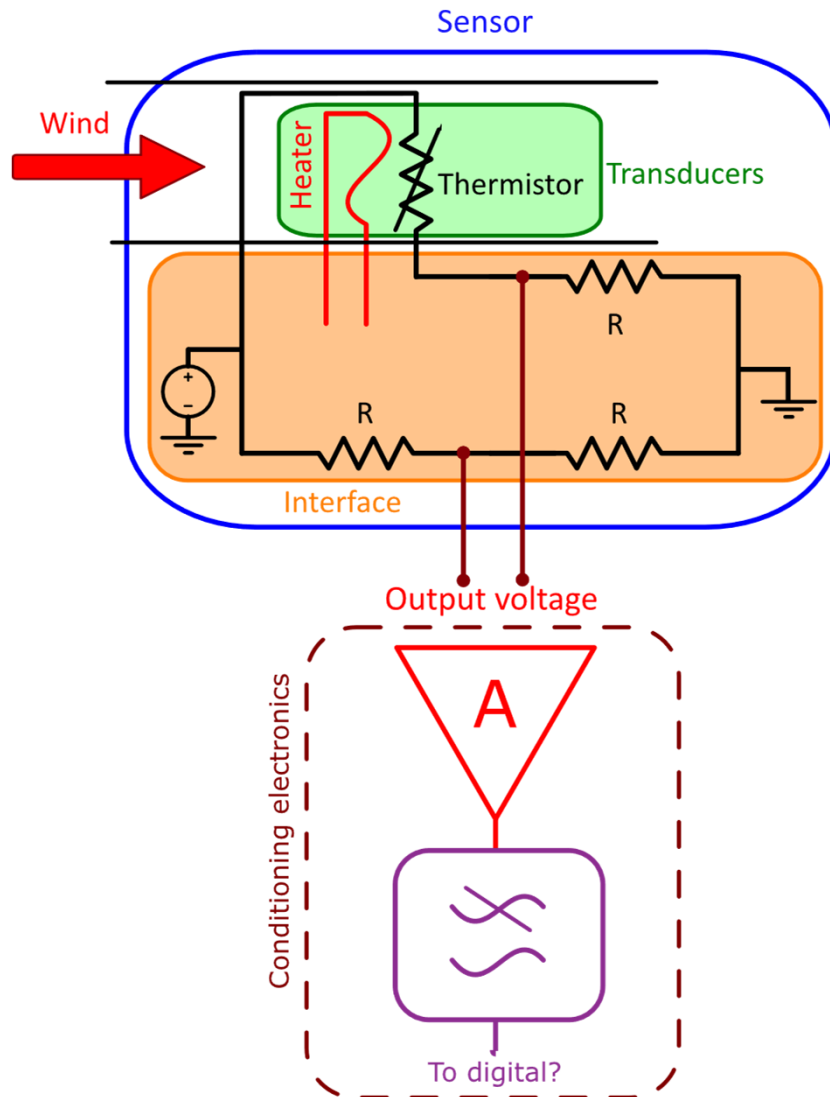


- A suitable sensor interface has to be able also to adapt itself to **different** kinds of both **sensors and measurands**, through appropriate electronic circuits, and to **improve signal processing** by suitable circuit design.
- The first stage of a sensor interface has to be **analog**, because of the analog nature of the signal coming from sensor.
- An electronic interface has the **dual task** to operate the **final transduction** in the case of a sensing element that does not produce a voltage or a current output, and **to manipulate** (amplify, filter etc...) the signal so to adapt it for the following stages.



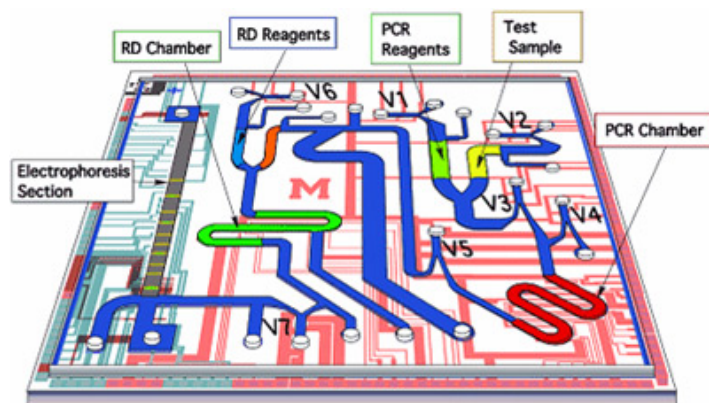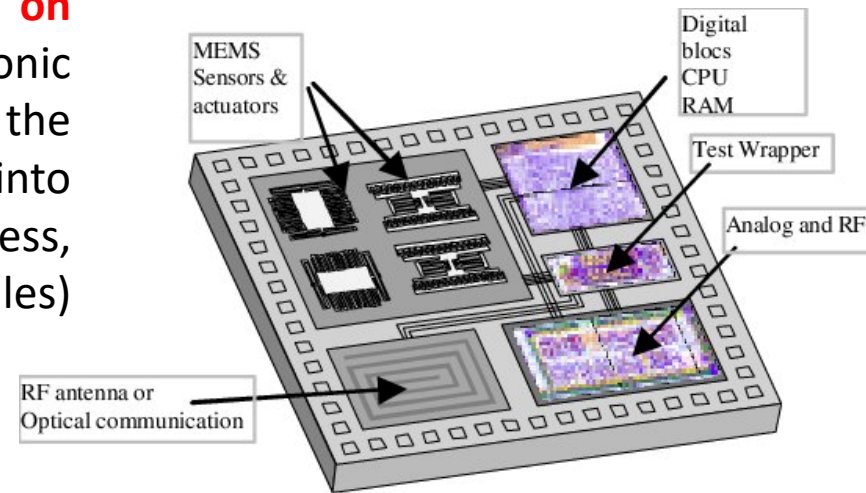
# Microsystems and micromodules

In **microsystems (System on Chip or Lab on Chip)** approach, sensor and electronic interface are integrated **on the same chip**, the microsensor has to be designed taking into account the material features (layer thickness, doping concentrations and design rules) imposed by the standard IC process used.



Obviously, this situation reduces the degrees of freedom available for sensor design, thus introducing additional challenges. Moreover, especially when using scaled-down (submicron) technologies, this approach can introduce **cost and yield problems**, but the advantage is related to **minimized and reproducible parasitics**.

# Microsystems and micromodules

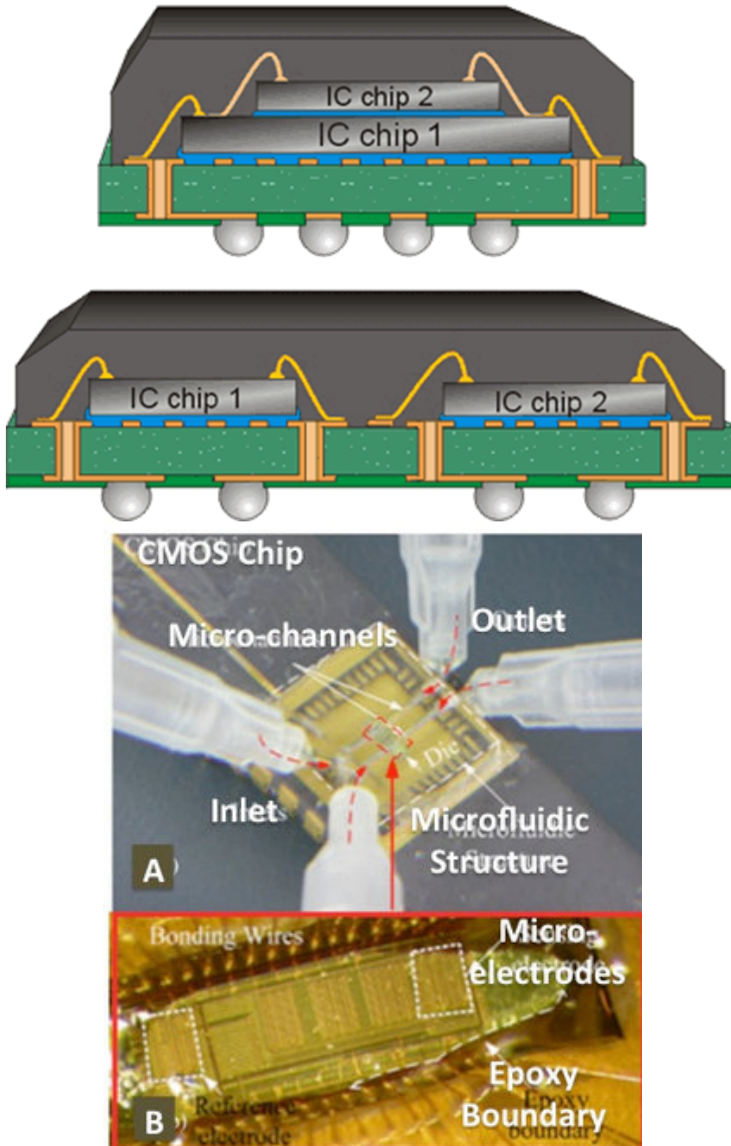


In **micromodule** approach the sensors and the electronic interface circuits are realized on **different chips**. They are included in the same package or mounted on the same substrate. Interconnections between the sensor and the electronic interface circuit chip can be realized with bonding wires or with other techniques, such as flip-chip or wafer bonding.

With this approach the two chips can be implemented with **different technologies**, optimized for the sensors and the circuitry, respectively. Typically, expensive submicron technologies are used to realize the electronic interface circuits, while low cost technologies with large feature size and few masks are used for implementing the sensors.

Drawbacks: large parasitics, difficult assembly, no matching.

# Micromodules and discrete approach

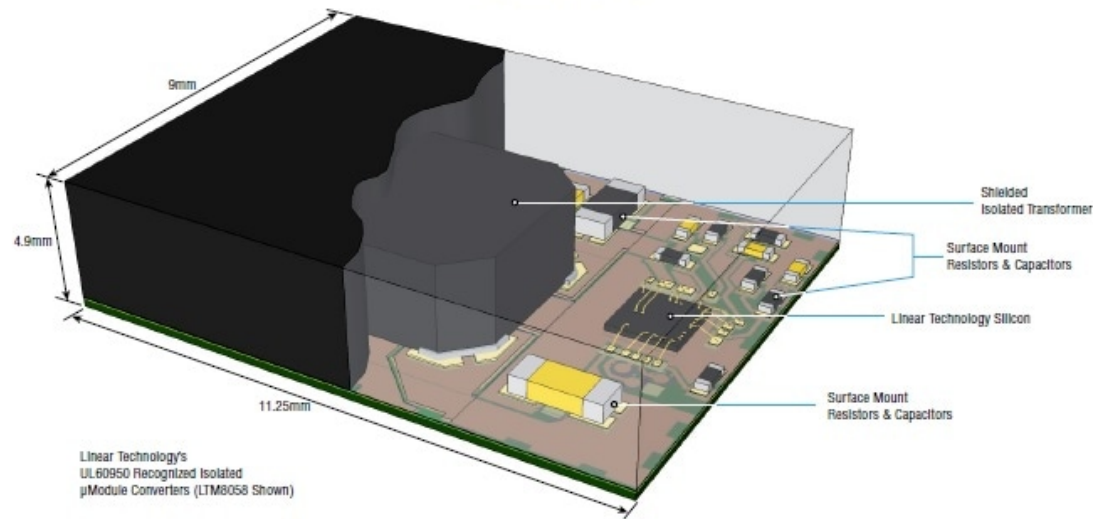

A micromodule can be also obtained by joining a **chip level sensor** with a **discrete level active device and passives**.



- Larger area occupation
- Larger parasitic components (lower frequency range)
- Higher power consumption



- Better testability and tunability
- Certainty of active device performances (datasheet)
- Improved time to develop



# CURRENT MODE READOUT APPROACH

# Introduction - a definition

---



*“A **voltage-mode** (VM) circuit is one whose signal states are completely and unambiguously determined by its node voltages; a **current-mode** (CM) circuit is one whose signal states are completely and unambiguously defined by its branch currents.”*

**B. Gilbert**

# Introduction - CM vs VM

---



For decades, the dominant signal representation mode has been in **voltage form**. Today it is much likely the same and it has to do also with **practical reasons**: voltages can readily be probed by instruments to be displayed and accurately measured without breaking circuit branches. In other words, **testing and validating** a circuit whose output is in the voltage form can be done in a **much easier** and accurate way.



Nonetheless, signaling in the **current mode** domain has its **benefits**, especially towards newer and very low pitch integrated technologies:

- **Higher sensitivity** circuits and interfaces with very much reduced supply voltages;
- very simple architectures are synthesizable;
- lower **power consumption** and higher bandwidths;
- capability to perform signal manipulations such as products, which in a purely VM approach would result extremely difficult.

# CM active devices
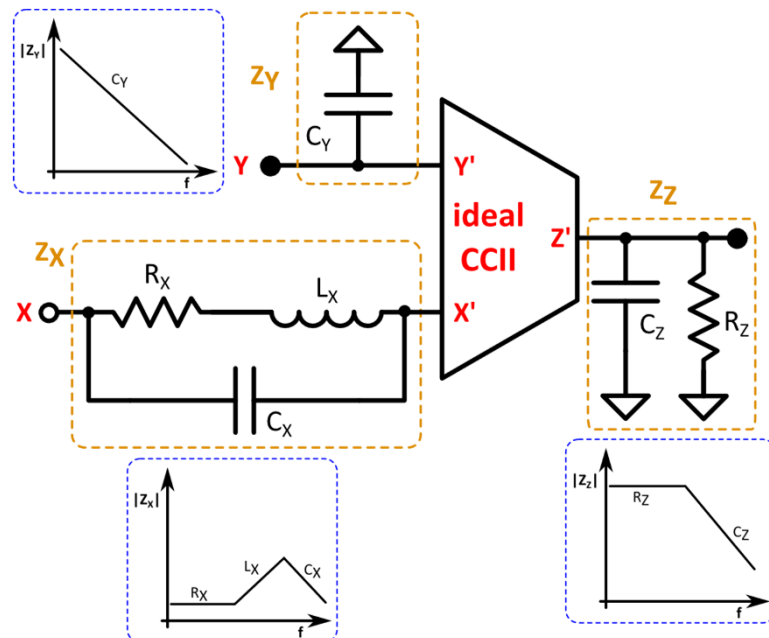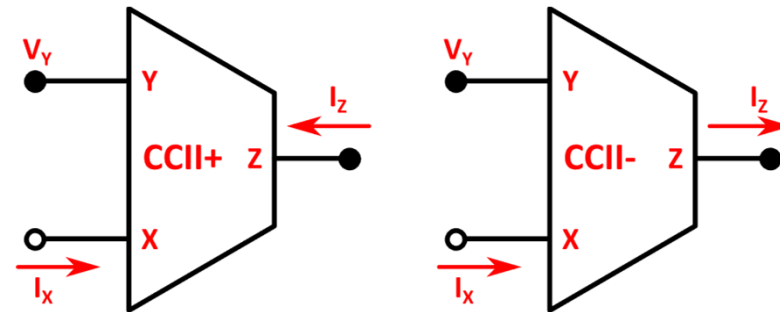
## SECOND GENERATION CURRENT CONVEYOR (CCII)

$$\begin{bmatrix} I_Y \\ V_X \\ I_Z \end{bmatrix} = \begin{bmatrix} sC_Y & 0 & 0 \\ \alpha & (R_X + sL_X) // \frac{1}{sC_X} & 0 \\ 0 & \pm\beta & \frac{1}{R_Z // \frac{1}{sC_Z}} \end{bmatrix} \begin{bmatrix} V_Y \\ I_X \\ V_Z \end{bmatrix}$$



- Well known current mode active device
- Low impedance current input at **X**
- High impedance voltage input at **Y**
- High impedance current output at **Z**
- Unitary  $\alpha$  and  $\beta$  parameters.  $\beta$  can be positive or negative.

The UnivAQ logo features the text "UnivAQ" in a dark grey, sans-serif font. The letters "A" and "Q" are significantly larger than the other letters. A yellow shield-like outline is positioned behind the "A" and "Q", with its top and bottom points extending above and below the letters respectively.

UnivAQ



# THE SECOND GENERATION VOLTAGE CONVEYOR (VCII)



# CM active devices
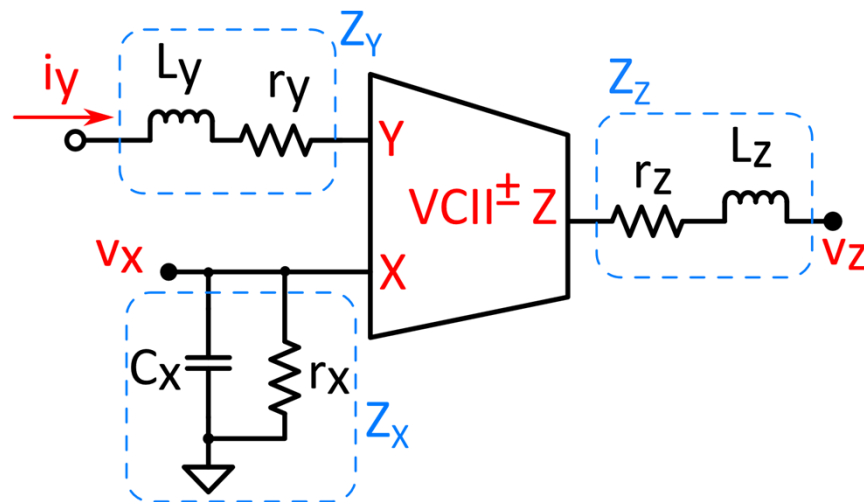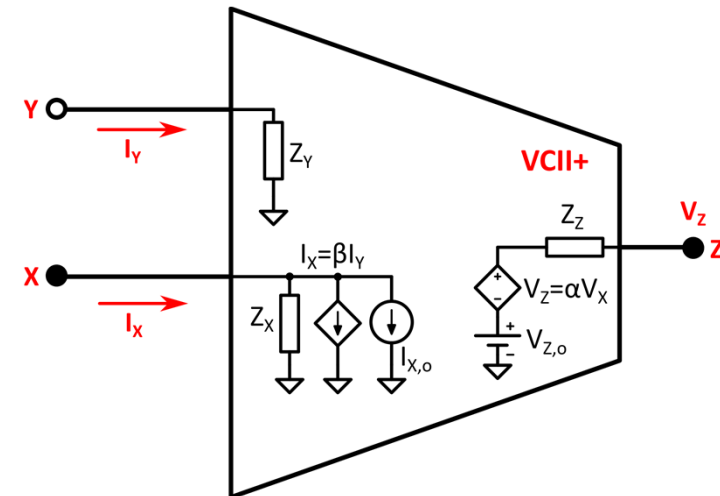
## SECOND GENERATION VOLTAGE CONVEYOR (VCII)

$$\begin{bmatrix} I_X \\ V_Y \\ V_Z \end{bmatrix} = \begin{bmatrix} \frac{1}{r_x} + sC_x & \pm\beta & 0 \\ 0 & r_y + sL_y & 0 \\ \alpha & 0 & r_z + sL_z \end{bmatrix} \begin{bmatrix} V_X \\ I_Y \\ I_Z \end{bmatrix}$$




- Relatively new current mode active device
- High impedance voltage input at **X**
- Low impedance current input at **Y**
- Low impedance **voltage output** at **Z**
- Unitary  $\alpha$  and  $\beta$  parameters.  $\beta$  can be positive or negative.
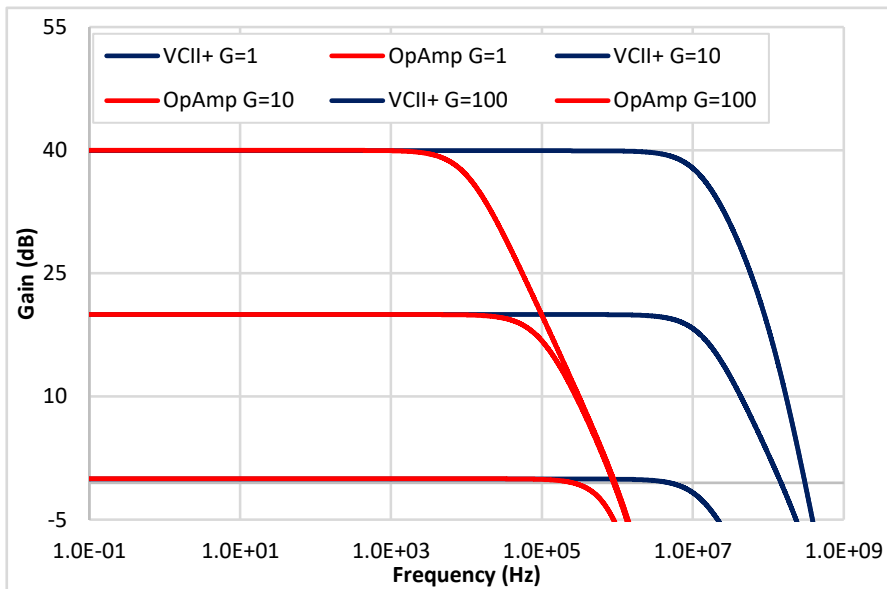
# A brief comparison

VCII <-> Op-Amp


The **voltage output** of a VCII can be a **linking point** between the voltage mode and the current mode approach.



- **Constant BW** at different gain levels
- Very easy transistor level topology
- Lower power consumption
- Higher GBW product due to the lack of frequency compensation



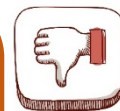
- No easy way to perform a differential measurement
- Impossibility to take advantage of the negative feedback properties




# A brief comparison

VCII  $\leftrightarrow$  CCII

CCII

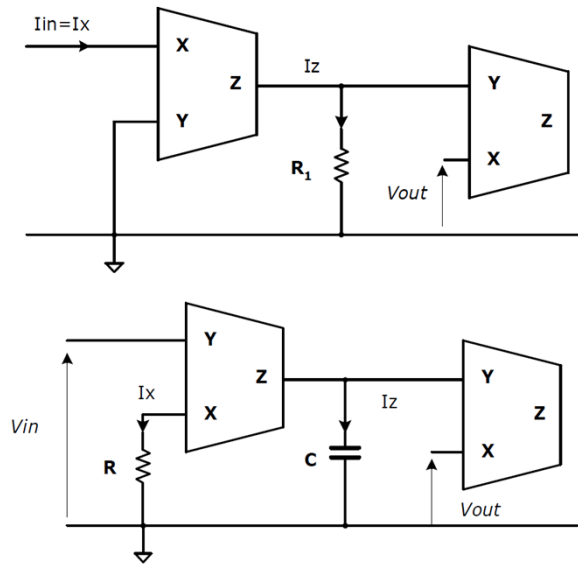

VCII

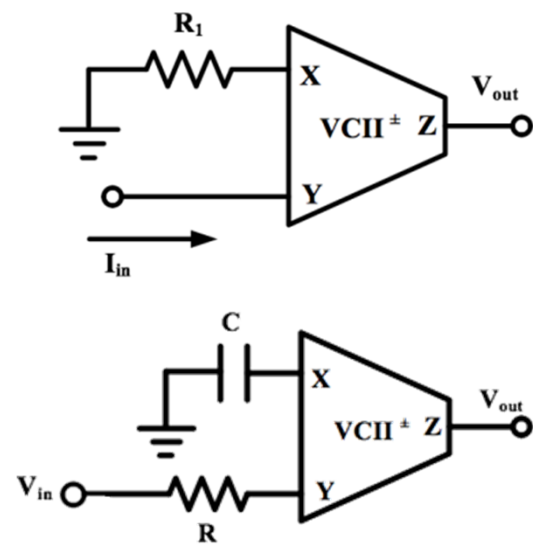

- Low impedance voltage output -> compatible with voltage mode systems
- Same signal processing capabilities with a **reduce number of active devices**


The UnivAQ logo features the text "UnivAQ" in a dark grey, sans-serif font. The letters "iv" are smaller and positioned to the left of "AQ". A yellow shield-like outline is positioned behind the text, with its top and bottom points extending above and below the "Q".

UnivAQ

# APPLICATION AS ANALOG INTERFACE

# Differential capacitive sensors


## Linear

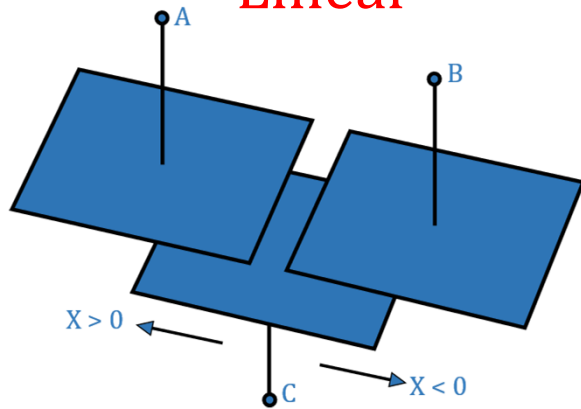

$$C_{1,2} = C_{bl}(1 \pm x)$$


$$(0 < C_{1,2} < 2C_{bl})$$

## Equivalent circuit

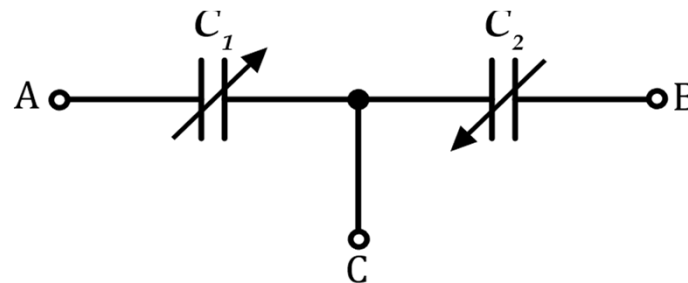

$$X = \frac{C_1 - C_2}{C_1 + C_2}$$

## Hyperbolic

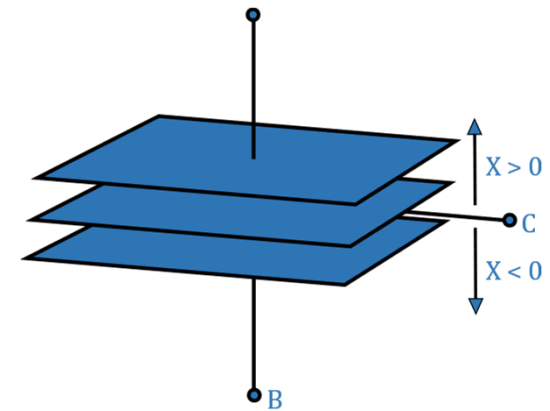


$$C_{1,2} = \frac{C_{bl}}{(1 \mp x)}$$

$$\left(\frac{C_{bl}}{2} < C_{1,2} < \infty\right)$$

- Couple of capacitors sharing a common node (C).
- Variations from a common baseline, in a differential way.

# Differential capacitive sensors

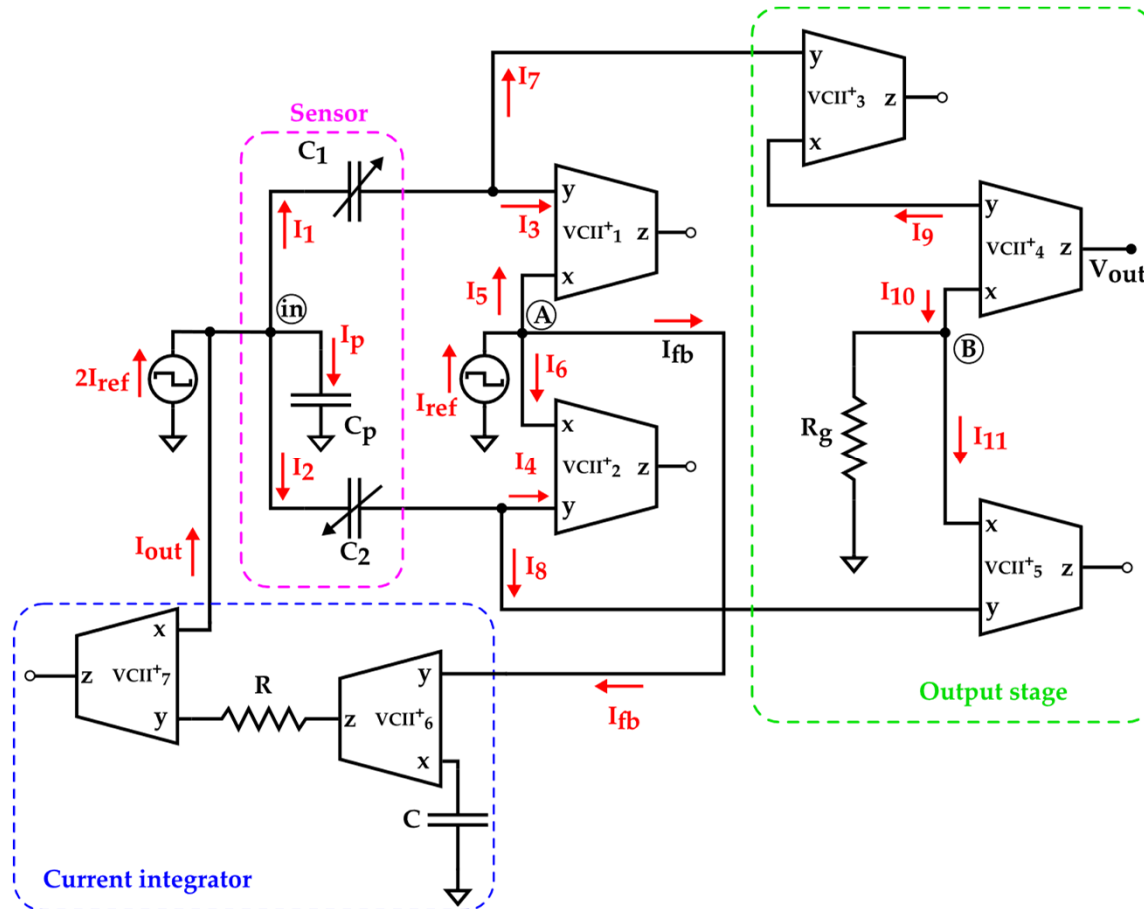


- **Output stage** performs the **difference** between currents flowing through the sensor
- **Time continuous current feedback** to compensate parasitic effects
- Tunable sensitivity either by increasing  $I_{ref}$  or  $R_g$

$$I_{out} = \alpha_7 \beta_7 \beta_8 \frac{1}{sRC} I_{fb}$$

$$V_{out} \approx \frac{R_g(I_1 - I_2)}{2} = R_g I_{ref} x$$



# Silicon photomultipliers (SiPMs)

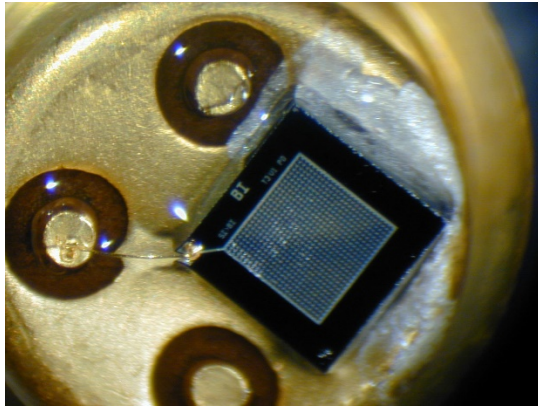


- Photomultipliers are **extremely sensitive detectors of light** (photons).
- The main role is to multiply the current produced by incident light up to 100 million times, in order to detect even individual photons.
- The **Silicon Photomultipliers**, or **SiPMs**, are much smaller than PMTs and can guarantee the same features, or even better performances in some cases.

**SiPMs structure:** series combination of an **avalanche photodiode (APD or SPAD)** with a **quenching resistor**.

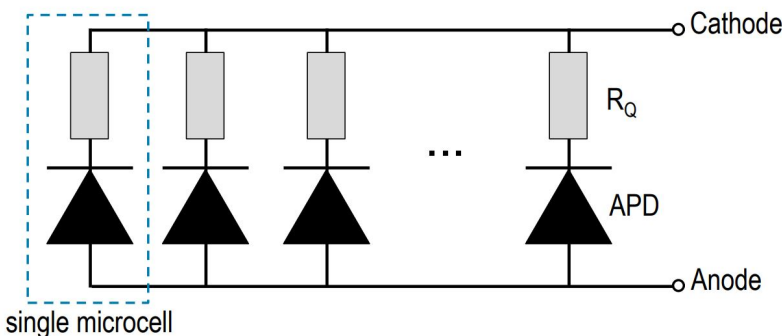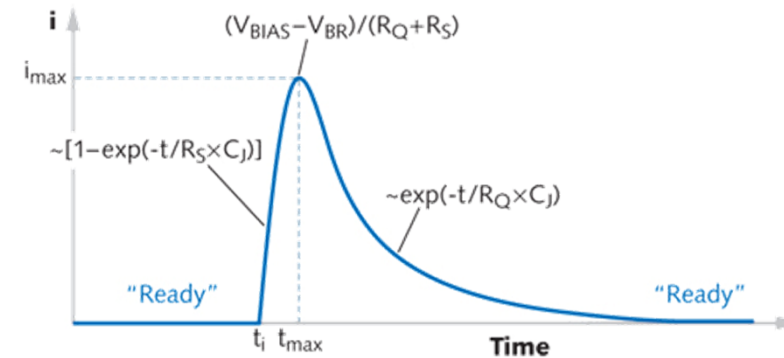**Biomedical applications:** optical sensors (Doppler, pulseoximeter etc...)





**Equivalent circuit model**

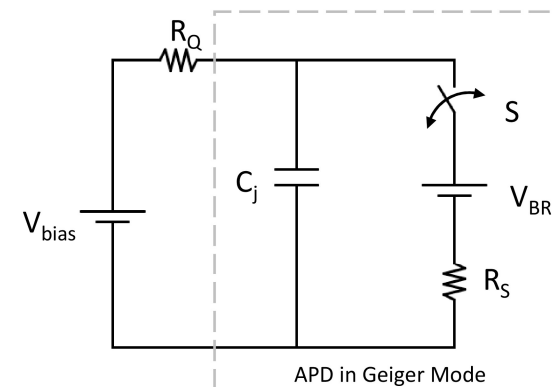
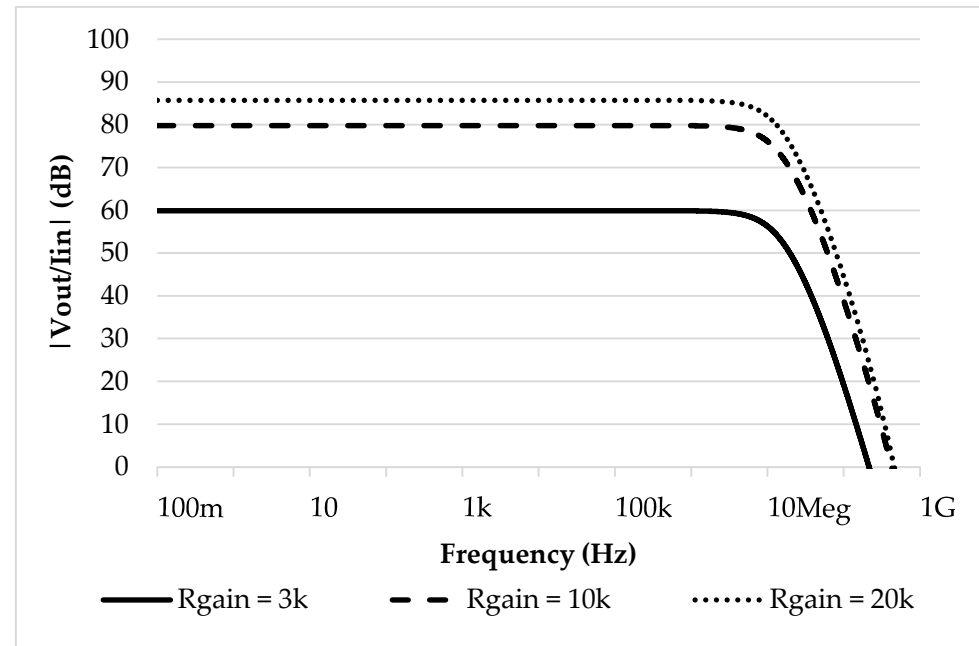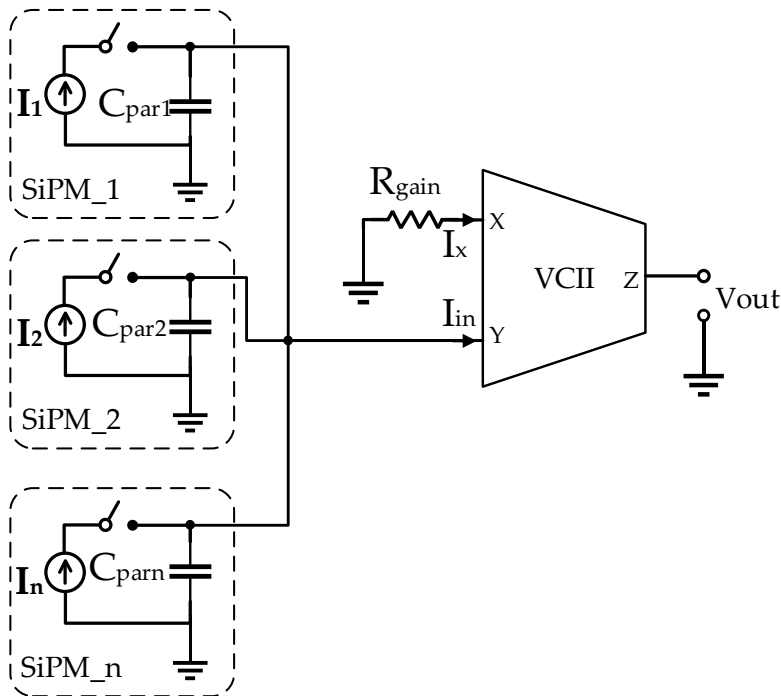
# The VCII as analog interface

- Due to its characteristics, the VCII can easily work as a **TI amplifier**.
- It can work for the **single SiPM** as well as an **array of SiPMs** without losing the information about how many photons hit the array.
- In the latter case the spatial information is lost.



$$V_x = I_x R_{gain} \approx \pm \beta I_{in} R_{gain}$$




$$V_{out} = \alpha V_x \approx \pm \alpha \beta R_{gain} I_{in} \approx R_{gain} I_{in}$$



# VCI TRANSISTOR LEVEL TOPOLOGIES

# Super transistor output stage

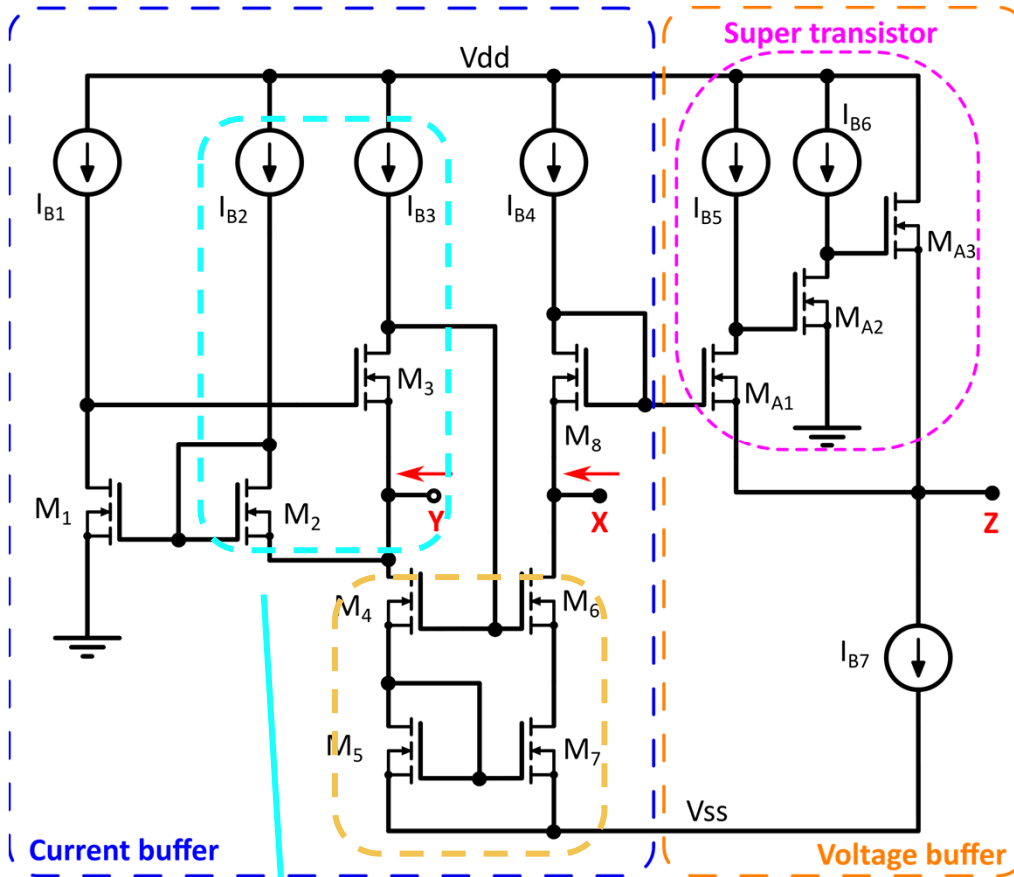

Regulated CG

Cascoded current mirror ( $\beta$ )


$$r_X = \frac{(r_{o7} + r_{o6} + g_{m6}r_{o6}r_{o7})(r_{o_{IB4}} + 1/g_{m8})}{(r_{o7} + r_{o6} + g_{m6}r_{o6}r_{o7} + r_{o_{IB4}} + 1/g_{m8})}$$

$$r_Y = \frac{1}{g_{m3}g_{m1}(r_{o1} \parallel r_{o_{IB1}}) g_{m'4}(r_{o_{IB3}} \parallel r_{o3})}$$

$$r_Z = \frac{1}{g_{m_{A1}}g_{m_{A2}}g_{m_{A3}}(r_{o_{A1}} \parallel r_{o_{IB5}})(r_{o_{A2}} \parallel r_{o_{IB6}})}$$

Parameter	Value
$r_x, C_x$	1.2M $\Omega$ , ~30fF
$r_y, L_y$	6.7 $\Omega$ , ~1.5 $\mu$ H
$r_z, L_z$	0.7 $\Omega$ , ~9 $\mu$ H
$\alpha$ (DC value, -3dB BW)	(0.997, 217MHz)
$\beta$ (DC value, -3dB BW)	(0.988, 200MHz)
Static Power Consumption	330 $\mu$ W (101 $\mu$ A)

# Translinear $\beta$ -tunable VCII

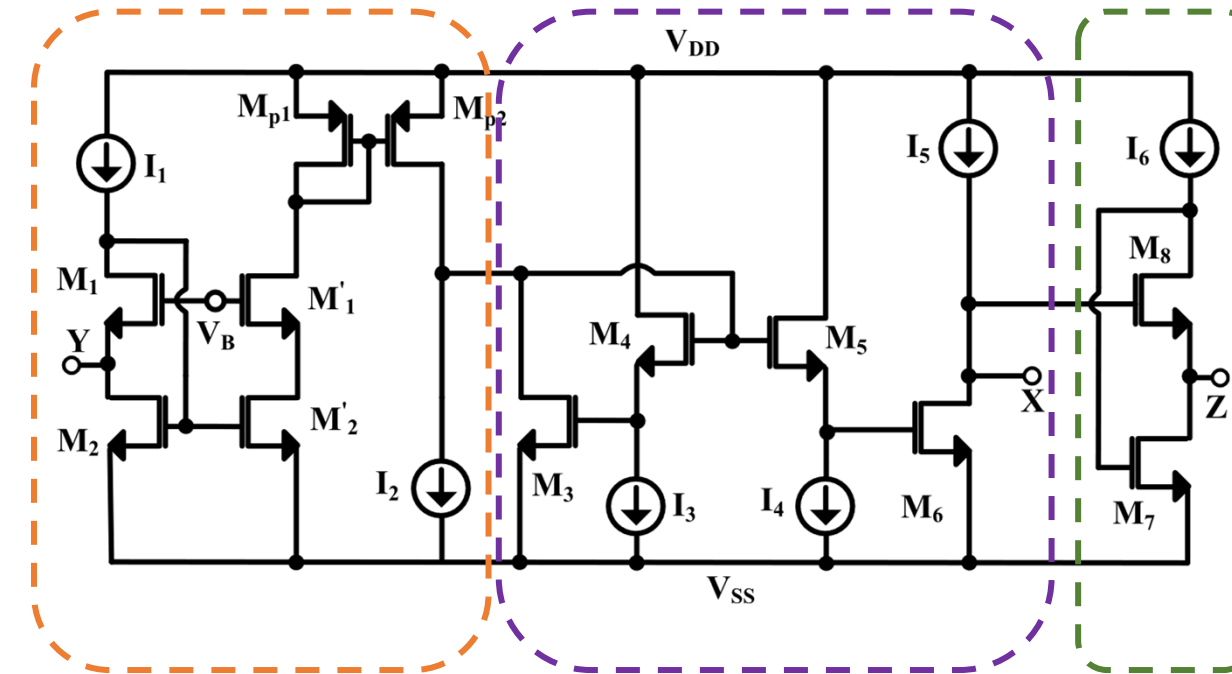

$$V_{GS3} + V_{GS4} = V_{GS1} + V_{GS2}$$

$$I = I_{D0} e^{\frac{V_{GS} - V_{TH}}{nU_T}}$$

$$I_3 I_4 = I_1 I_2$$

Flipped voltage follower

Current mirroring

Translinear Core

- Based on the **translinear theory** => a **PROPER CM device**
- Exponential relationship between  $I_d$  and  $V_{gs}$  needed
- **Weak inversion** biased transistors -> extremely low power consumption
- Flipped voltage follower output, suitable for weak inversion operations.

$$G = \frac{I_X}{I_Y} = \frac{I_3}{I_4}$$

**END OF PRESENTATION**

---



**THANK  
YOU!**